



$$V_{IN} = I(R + j\omega L)$$

$$I = \frac{V_{IN}}{R + j\omega L}$$


$$V_{OUT} = IR$$

$$= \left(\frac{V_{IN}}{R + j\omega L} \right) R$$

$$H(\omega) = \frac{V_{OUT}}{V_{IN}} = \frac{1}{V_{IN}} \left(\frac{V_{IN}}{R + j\omega L} \right) R$$

$$= \frac{R}{R + j\omega L} \quad \text{Plot in Maple}$$

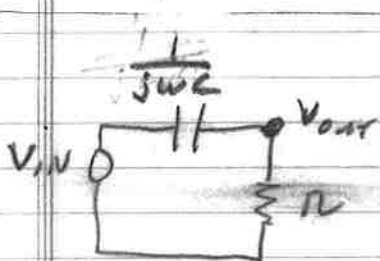* Let $R = 1 \text{ k}\Omega$ and plot $H(\omega)$
 $L = 0.1 \text{ H}$



$$V_{IN} = I \left(R + \frac{1}{j\omega C} \right)$$

$$I = \frac{V_{IN}}{R + \frac{1}{j\omega C}}$$

$$V_{OUT} = IR$$

$$= \left(\frac{V_{IN}}{R + \frac{1}{j\omega C}} \right) R$$

$$H(\omega) = \frac{V_{OUT}}{V_{IN}} = \frac{1}{V_{IN}} \left(\frac{V_{IN}}{R + \frac{1}{j\omega C}} \right) R$$

$$= \frac{R}{R + \frac{1}{j\omega C}}$$

* Let $R = 1 \text{ k}\Omega$ and plot $H(\omega)$
 $C = 4.7 \mu\text{F}$



$$V_{IN} = I \left(R + j\omega L + \frac{1}{j\omega C} \right)$$

$$I = \frac{V_{IN}}{R + j\omega L + \frac{1}{j\omega C}}$$

* BAND PASS, RLC

$$V_{OUT} = I R$$

$$= R \left(\frac{V_{IN}}{R + j\omega L + \frac{1}{j\omega C}} \right)$$

$$H(\omega) = \frac{V_{OUT}}{V_{IN}} = \frac{1}{V_{IN}} \left(\frac{V_{IN}}{R + j\omega L + \frac{1}{j\omega C}} \right) R$$

$$= \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

* Let $\begin{cases} R = 1 \text{ k}\Omega \\ L = 0.1 \text{ H} \\ C = 4.7 \mu\text{F} \end{cases}$


and plot in Maple

W. F.

* NOTES: $[R] = \left[\frac{V}{I} \right] = \frac{V}{A} = \frac{V/C}{C/s} = \frac{V \cdot s}{C^2} = \Omega$

$$[j\omega L] = \frac{1}{\text{sec}} \cdot \text{H} = \left(\frac{1}{s} \right) \left(\frac{V \cdot s^2}{C} \right) = \frac{V \cdot s}{C^2} = \Omega$$
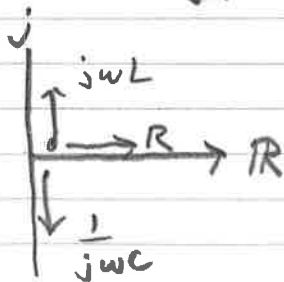
$$-\frac{j}{\omega C} = \frac{j}{j\omega C} = \frac{1}{j\omega C}, \quad \left[\frac{1}{j\omega C} \right] = \frac{1}{\frac{1}{s} \cdot F} = \frac{s}{C^2/s} = \frac{V \cdot s}{C^2} = \Omega$$



with(plots) :

$$R := 1000 \ \Omega$$

$$1000 \quad (1)$$

$$C := 4.7e-6 \ \text{F}$$

$$0.0000047 \quad (2)$$

$$L := .1 \ \text{H}$$

$$0.1 \quad (3)$$

$$H1 := \frac{R}{\left(\frac{1}{I \cdot \omega \cdot C} + R\right)}$$

$$\frac{1000}{-\frac{2.127659574 \cdot 10^5 I}{\omega} + 1000} \quad (4)$$


$$H2 := \frac{R}{(I \cdot \omega \cdot L + R)}$$

$$\frac{1000}{0.1 I \omega + 1000} \quad (5)$$


$$H3 := \frac{R}{\left(I \cdot \omega \cdot L + \left(\frac{1}{I \cdot \omega \cdot C}\right) + R\right)}$$

$$\frac{1000}{0.1 I \omega - \frac{2.127659574 \cdot 10^5 I}{\omega} + 1000} \quad (6)$$


plot(abs(H1), w = 0 .. 300 · π)

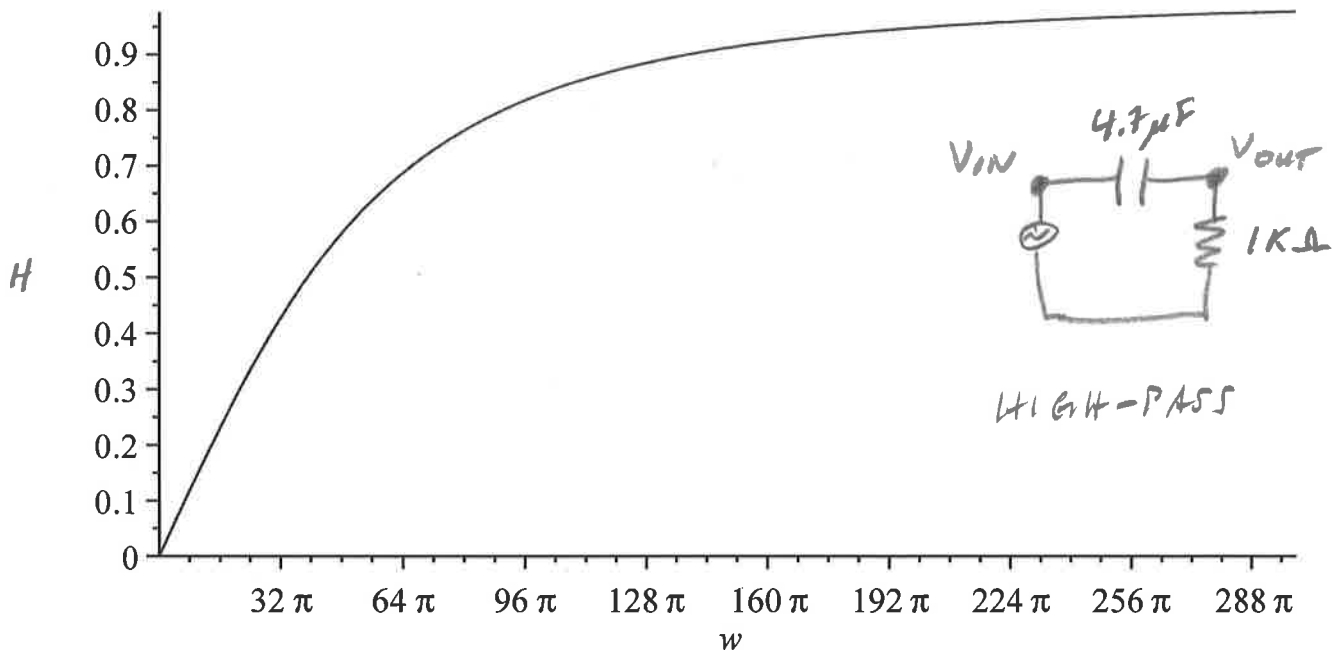

plot(abs(H2), w = 0 .. 3000 · π)

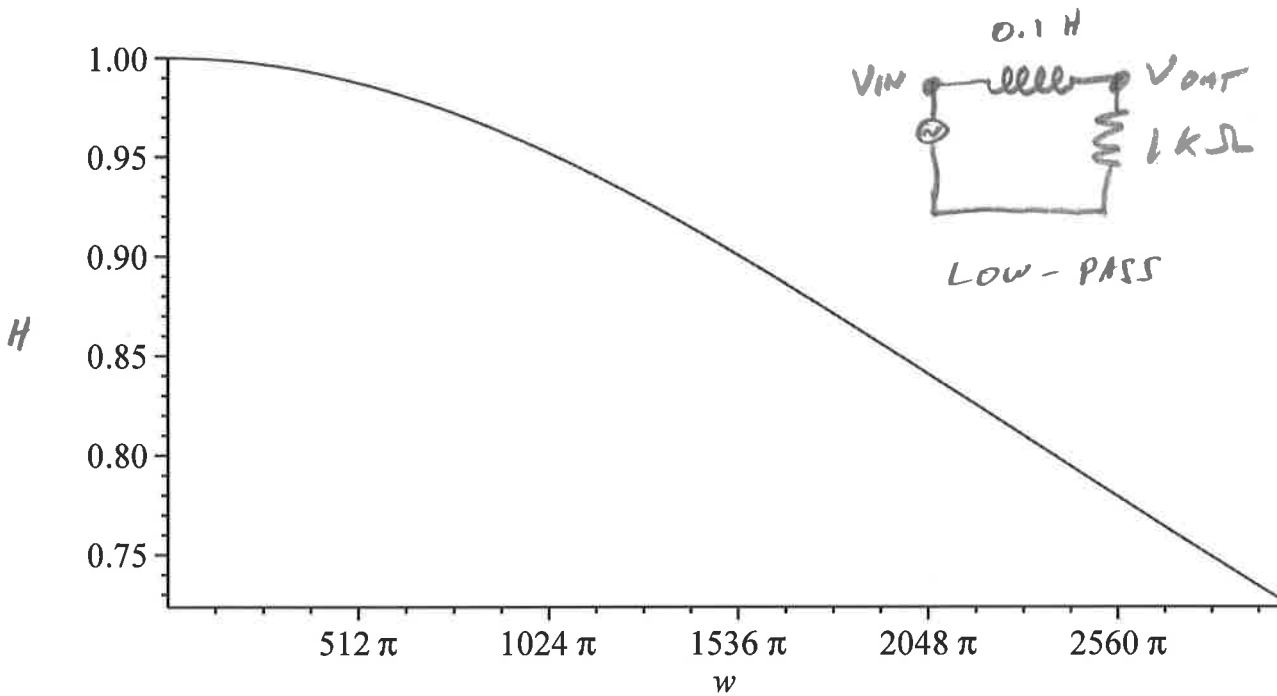

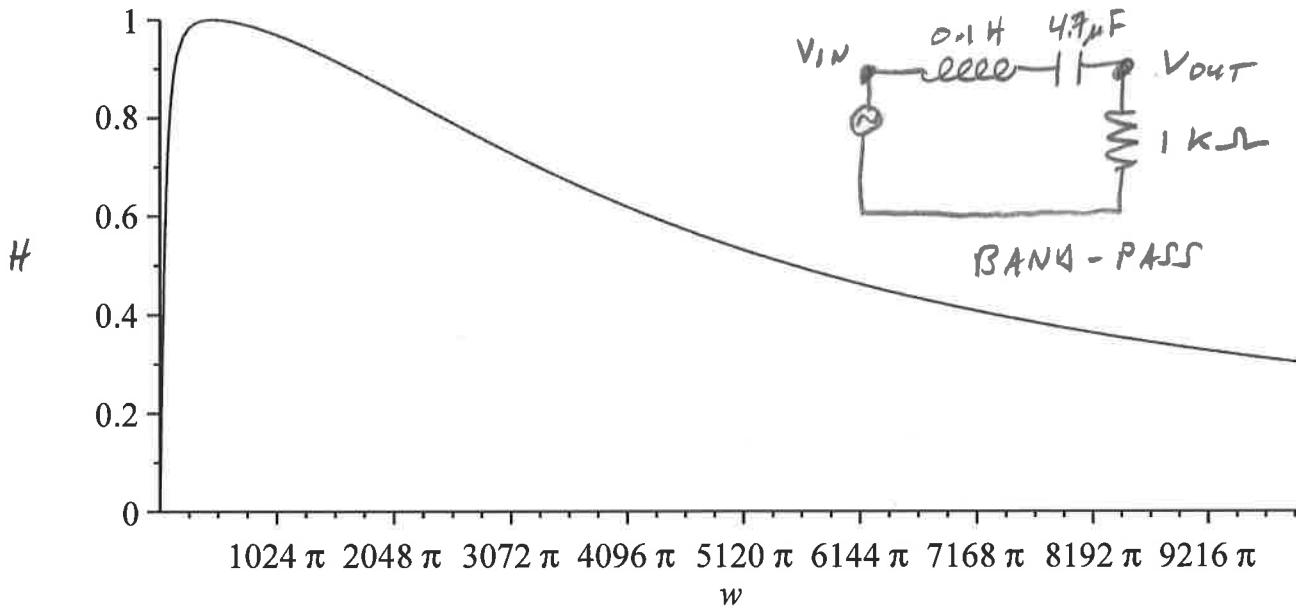$\text{plot}(\text{abs}(H3), w = 0..10000 \cdot \pi)$



$$A := \frac{1}{(\sqrt{L \cdot C})}$$

$$\omega_R = 1458.649915 \text{ rad/s} \quad (7)$$

$$\frac{A}{(2 \cdot 3.14159)}$$

$$f_R = 232.1515403 \text{ Hz} \quad (8)$$